

**UNIVERSITY COLLEGE TATI (UC TATI)**

FINAL EXAMINATION QUESTION BOOKLET		
COURSE CODE	:	DEI 1013
COURSE	:	ELECTRONICS
SEMESTER / SESSION	:	01 - 2024/2025
DURATION	:	3 HOURS

**Instructions:**


1. This booklet contains **4** questions. Answer **ALL**.
2. All answers should be written in the answer booklet.
3. Write legibly and draw sketches wherever required.
4. If in doubt, raise your hand and ask the invigilator.

**DO NOT OPEN THIS BOOKLET UNTIL YOU ARE TOLD TO DO SO**

**THIS BOOKLET CONTAINS 6 PRINTED PAGES INCLUDING COVER PAGE**


**QUESTION 1**

a) The application of the diode in the rectifier circuit is shown in **Figure 1**.

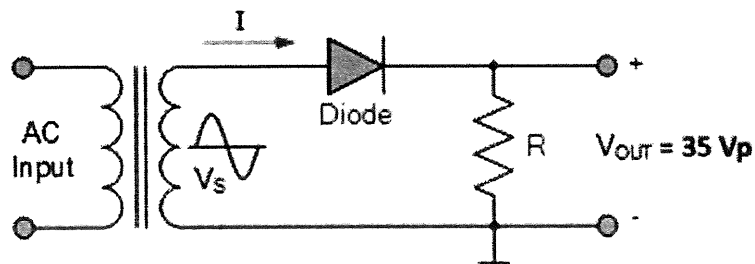**Figure 1**


- i. State the name of the circuit. (2 marks)
- ii. Give the function of the diode. (2 marks)
- iii. Calculate the average voltage  $V_{AVG}$ . (4 marks)
- iv. Calculate the rms voltage  $V_{rms}$ . (4 marks)

b) Refer to the rectifier circuit in **Figure 2**.

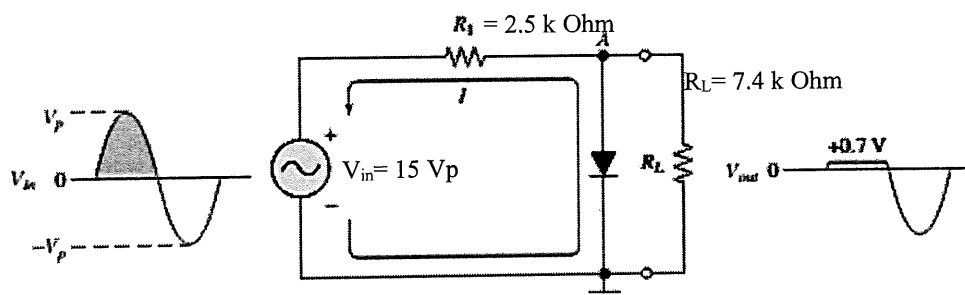**Figure 2**

- i. State the name of the circuit. (2 marks)
- ii. Compute the output voltage  $V_{out}$ . (4 marks)

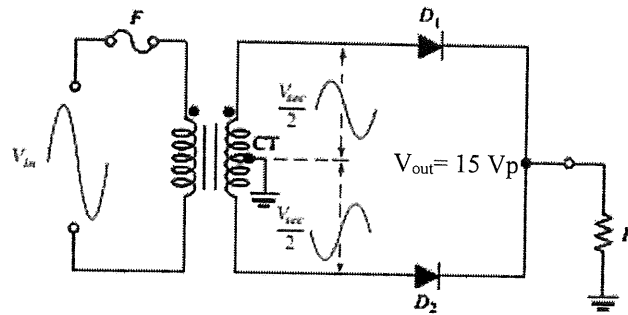c) The application of the diode in the rectifier circuit is shown in **Figure 3**.

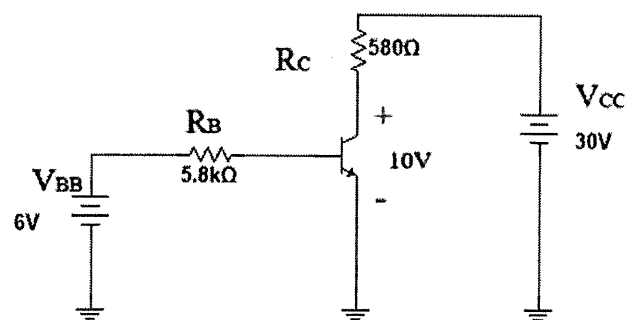


**Figure 3**

- i. State the name of the circuit. (2 marks)
- ii. Calculate the average voltage  $V_{AVG}$ . (4 marks)
- iii. Calculate the rms voltage  $V_{rms}$ . (4 marks)

**QUESTION 2**

- a) Define a transistor. (3 marks)
- b) List the three (3) DC biasing circuits of a Bipolar Junction Transistor (BJT). (3 marks)
- c) Give the three (3) states of BJT operation. (3 marks)
- d) Draw the basic construction of an NPN BJT transistor. (6 marks)
- e) Based on the BJT amplifier circuit as shown in **Figure 4**:

**Figure 4**


- i) Calculate the base current,  $I_B$ . (4 marks)
- ii) Calculate the collector current,  $I_C$ . (4 marks)
- iii) Calculate the emitter current,  $I_E$ . (4 marks)

**QUESTION 3**

a) Explain the purpose of dc biasing of a transistor.

(3 marks)

b) Based on the common-emitter amplifier circuit shown in **Figure 5**:  
Given  $\beta = 120$ .

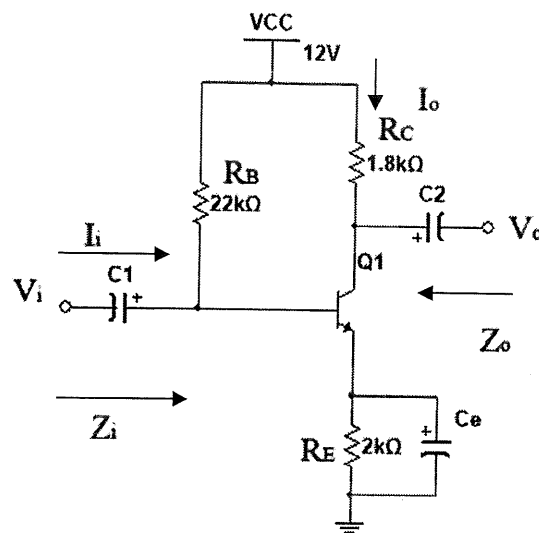

**Figure 5**

i) Explain the function of coupling capacitors  $C_1$  and  $C_2$  in the circuit.

(4 marks)

ii) Calculate the base current,  $I_B$ .

(4 marks)

iii) Calculate the emitter current,  $I_E$ .

(4 marks)

iv) Calculate the emitter resistance,  $r_e$ .

(4 marks)

v) Calculate the input impedance,  $Z_i$ .


(4 marks)

vi) Calculate the output impedance,  $Z_o$ .

(4 marks)

**QUESTION 4**

- a) The most commonly used audio amplifier classes are A, B, AB, and C.
- Illustrate the input and output signal waveforms of the class A amplifier. (4 marks)
  - Illustrate the input and output signal waveforms of the class B amplifier. (4 marks)
- b) Based on the circuit in **Figure 6**, state the name of the amplifier class. (1 mark)

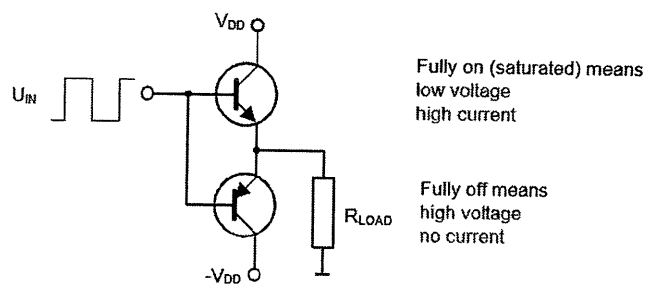**Figure 6**

- Define a regulator. (4 marks)
- Describe the unregulated power supply. (5 marks)

-----End of Questions-----