



**UNIVERSITY COLLEGE TATI (UC TATI)**

**FINAL EXAMINATION QUESTION BOOKLET**

COURSE CODE : DEE 1113

COURSE : ELECTRICAL TECHNOLOGY I

SEMESTER/SESSION : 1-2024/2025

DURATION : 3 HOURS

**Instructions:**

1. This booklet contains 4 questions. Answer **ALL** the questions.
2. All answers should be written in answer booklet.
3. Write legibly and draw sketches wherever required.
4. If in doubt, raise your hands and ask the invigilator.

**DO NOT OPEN THIS BOOKLET UNTIL YOU ARE TOLD TO DO SO**

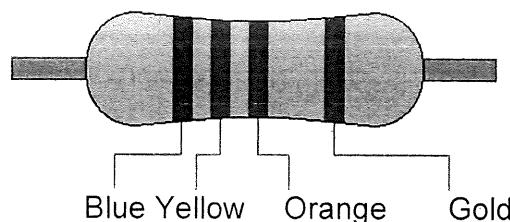
**THIS BOOKLET CONTAINS 10 PRINTED PAGES INCLUDING COVER PAGE**

**QUESTION 1**

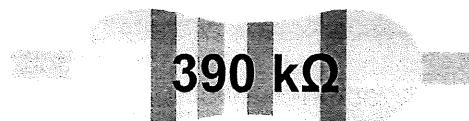
- a) Current consists of two types which are direct current (DC) and alternating current (AC).  
Draw both current waveform types. (4 marks)
- b) Express each of the following numbers in **scientific notation**.  
(i) 0.0046 (2 marks)  
(ii)  $780000000 + 680000$  (3 marks)
- c) Express each of the following numbers in **engineering notation** and **SI prefix** form.  
(i) 13 000000 (4 marks)  
(ii) 0.00000149 (4 marks)
- d) Compute the **coulombs of charge** do  $40 \times 10^{30}$  electrons possess. (4 marks)

**QUESTION 2**

- a) Draw symbol of resistor. (1 mark)
- b) State THREE (3) factors determined the resistance of any material. (3 marks)
- c) Figure 1 shows a 4 band resistor.

**Figure 1**

- i) Determine the resistance values and tolerance for the following 4-band resistor. (2 marks)
- ii) Find the minimum and the maximum resistance within the tolerance limits for the resistor in c) (i). (5 marks)
- d) Determine the color bands for the 4 band resistor in Figure 2. Assume it has a 10% tolerance. (2 marks)

**Figure 2**

- e) Express the resistance value in ohm ( $\Omega$ ) indicated in Figure 3. (1 mark)

**Figure 3**

- f) Compute the **current**,  $I$  in the circuit in Figure 4. (3 marks)

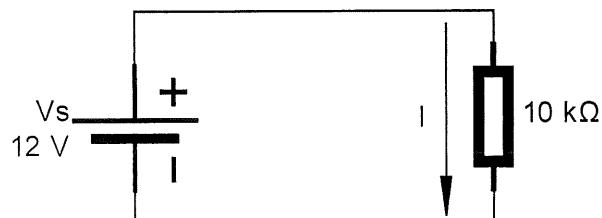


Figure 4

- g) An electric heater works by passing a current of 100 A though a coiled metal wire, making it red hot. If the resistance of the wire is  $2.4\ \Omega$ , determine **voltage** must be applied to it.

(3 marks)

- h) Determine the **power** value does the resistor,  $R$  in Figure 5 dissipate. (3 marks)

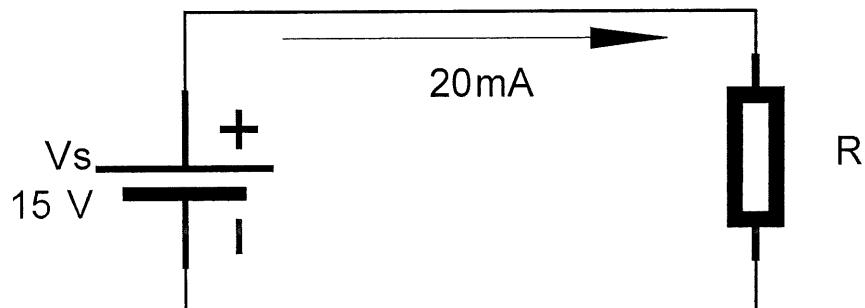
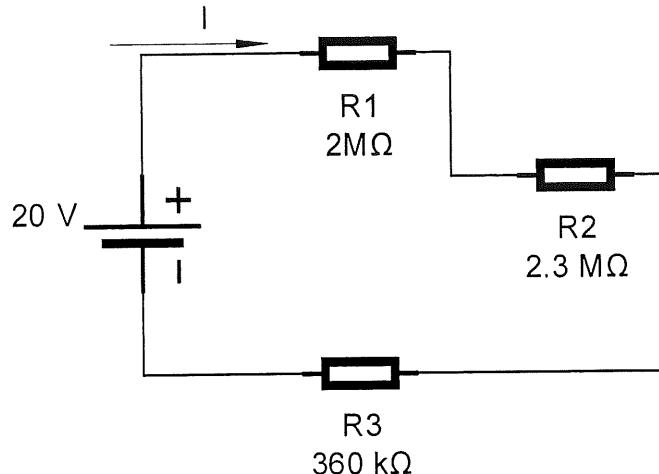


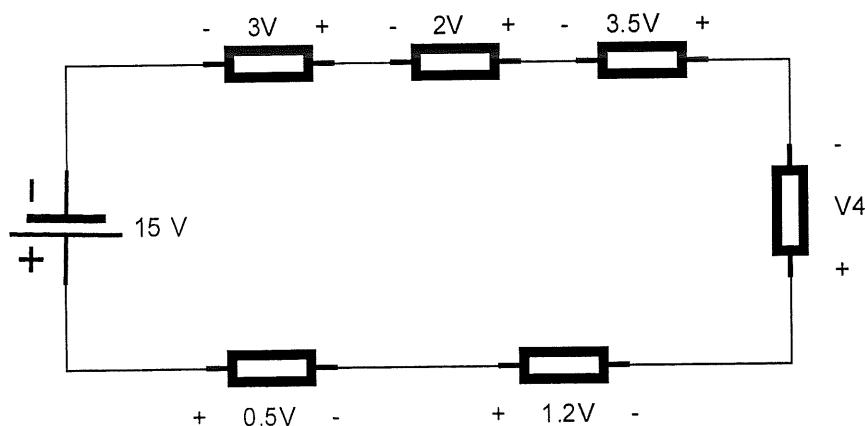
Figure 5

**QUESTION 3**


- a) For the circuit in Figure 6, calculate:

**Figure 6**

- (i) Total resistance of the circuit. (3 marks)
  - (ii) Current,  $I$  flow in the circuit. (3 marks)
  - (iii) Voltage across  $R_2$ . (3 marks)
- b) Determine voltage drop at  $V_4$  in Figure 7 using Kirchhoff's Voltage Law. (2 marks)


**Figure 7**

- c) For the voltage divider circuit shown in Figure 8;

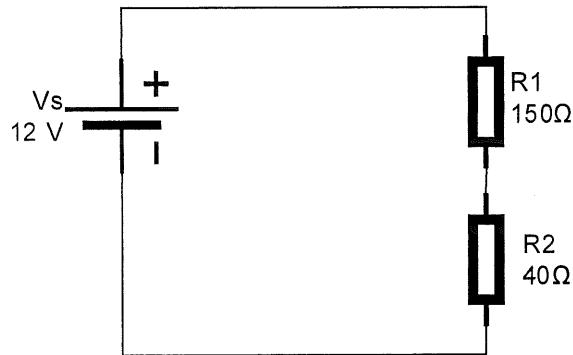

**Figure 8**

- (i) Express the voltage across  $R_2$  using voltage divider formula. (4 marks)
  - (ii) Calculate the total power in the circuit. (4 marks)
- d) For the circuit in Figure 9;

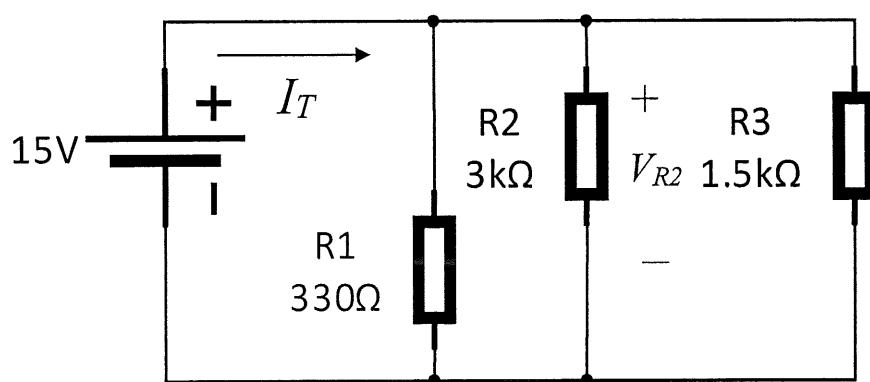


**Figure 9**

- (i) Compute total resistance,  $R_T$  of the circuit. (3 marks)
- (ii) Determine total current,  $I_T$ . (3 marks)
- (iii) Express voltage at  $R_2$ ,  $V_{R2}$ . (2 marks)


**QUESTION 4**

- a) Find the capacitance when  $Q = 50 \mu\text{C}$  and  $V = 10 \text{ V}$ . (3 marks)

- b) For the circuit in Figure 10;

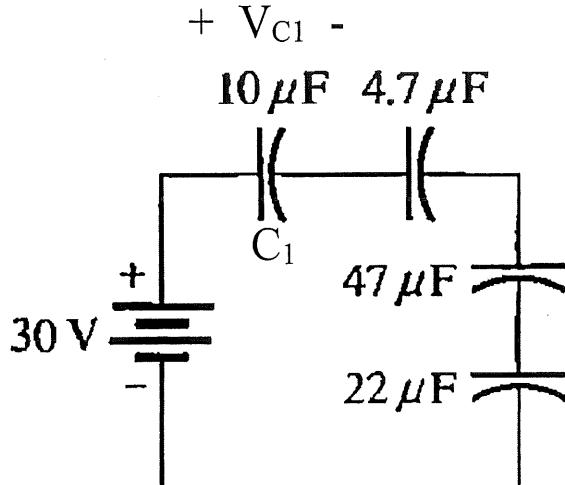**Figure 10**

- (i) Compute the total capacitance for the circuit,  $C_T$ . (3 marks)  
(ii) Calculate the voltage across  $C_1$ ,  $V_{C1}$ . (3 marks)
- c) Figure 11 shows a parallel connection of capacitors.

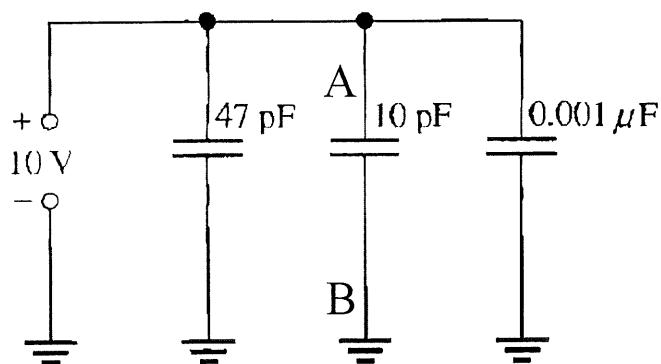**Figure 11**

- (i) Calculate the total capacitance for the circuit,  $C_T$ . (3 marks)  
(ii) Determine the voltage across point A and B. (2 marks)

- d) Find the amount of energy stored in a 4.7 mH inductor when the current is 2 A.  
(3 marks)
- e) A student wraps 100 turns of wire on a pencil that is 0.007m in a diameter as shown in Figure 12. The pencil has the same permeability as a vacuum ( $4\pi \times 10^{-6}$  H/m). Find the **inductance**, L of the coil that is formed.  
(3 marks)

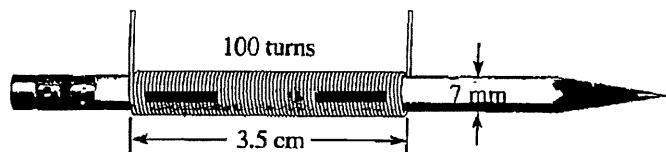


Figure 12

- f) Compute the **total inductance**,  $L_T$  for Figure 13 and Figure 14.

(i) (2 marks)

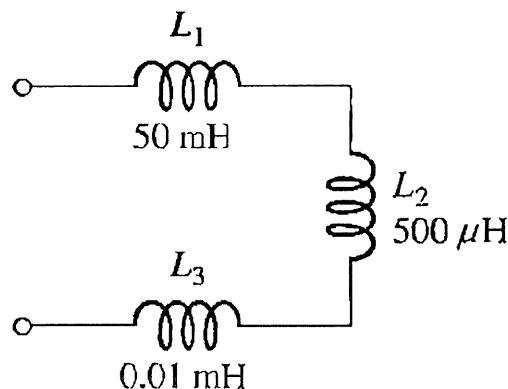


Figure 13

(ii) (4 marks)

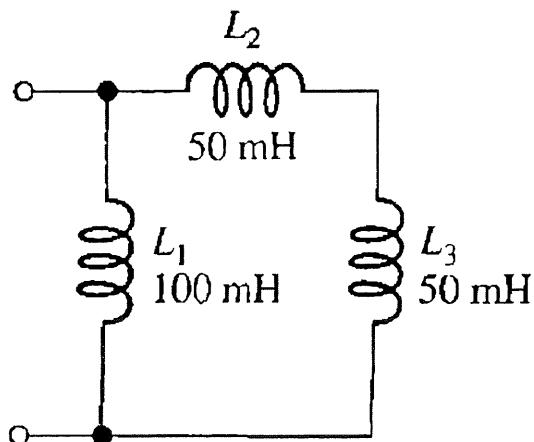


Figure 14

g) Determine the time constant,  $\tau$  for the series of RL combinations as in the Figure 15.

(3 marks)

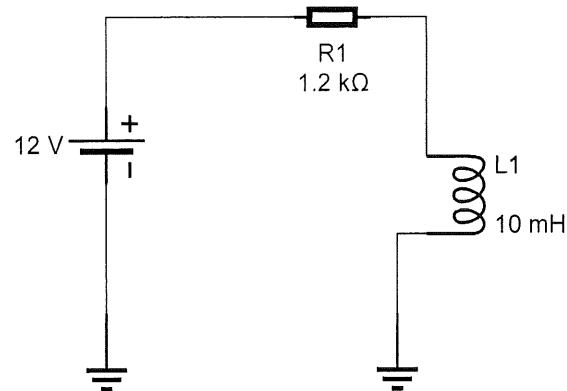


Figure 15

-----End of question-----

## Appendix

$Q = \frac{\text{number of electron}}{6.25 \times 10^{18} e / C}$	<table border="1"> <thead> <tr> <th>Color</th><th>Value</th><th>Multiplier</th><th>Tolerance</th></tr> </thead> <tbody> <tr> <td>Black</td><td>0</td><td><math>\times 10^0</math></td><td><math>\pm 20\%</math></td></tr> <tr> <td>Brown</td><td>1</td><td><math>\times 10^1</math></td><td><math>\pm 1\%</math></td></tr> <tr> <td>Red</td><td>2</td><td><math>\times 10^2</math></td><td><math>\pm 2\%</math></td></tr> <tr> <td>Orange</td><td>3</td><td><math>\times 10^3</math></td><td><math>\pm 3\%</math></td></tr> <tr> <td>Yellow</td><td>4</td><td><math>\times 10^4</math></td><td><math>-0,+100\%</math></td></tr> <tr> <td>Green</td><td>5</td><td><math>\times 10^5</math></td><td><math>\pm 0.5\%</math></td></tr> <tr> <td>Blue</td><td>6</td><td><math>\times 10^6</math></td><td><math>\pm 0.25\%</math></td></tr> <tr> <td>Violet</td><td>7</td><td><math>\times 10^7</math></td><td><math>\pm 0.10\%</math></td></tr> </tbody> </table>	Color	Value	Multiplier	Tolerance	Black	0	$\times 10^0$	$\pm 20\%$	Brown	1	$\times 10^1$	$\pm 1\%$	Red	2	$\times 10^2$	$\pm 2\%$	Orange	3	$\times 10^3$	$\pm 3\%$	Yellow	4	$\times 10^4$	$-0,+100\%$	Green	5	$\times 10^5$	$\pm 0.5\%$	Blue	6	$\times 10^6$	$\pm 0.25\%$	Violet	7	$\times 10^7$	$\pm 0.10\%$
Color	Value	Multiplier	Tolerance																																		
Black	0	$\times 10^0$	$\pm 20\%$																																		
Brown	1	$\times 10^1$	$\pm 1\%$																																		
Red	2	$\times 10^2$	$\pm 2\%$																																		
Orange	3	$\times 10^3$	$\pm 3\%$																																		
Yellow	4	$\times 10^4$	$-0,+100\%$																																		
Green	5	$\times 10^5$	$\pm 0.5\%$																																		
Blue	6	$\times 10^6$	$\pm 0.25\%$																																		
Violet	7	$\times 10^7$	$\pm 0.10\%$																																		
$I = \frac{Q}{t}$																																					
$P = V \times I$																																					
$P = V^2 \div R$																																					
$P = I^2 \times R$																																					
$V = W \div Q$																																					
$R = p l/A \Omega$																																					
$V = IR$																																					
$L = \frac{N^2 \mu A}{l}$																																					
$W = \frac{1}{2} L I^2$																																					
$\tau = L/R$																																					